

ON 796	Si-N	≈BC 548			≈BC 548	
ON 974	Si-N	≈BU 508	18j		BU 2508 A	18j
ON 1128	Opto	Opto-Koppler/coupler			-	
ON 4046	Si-N	≈S 2000A, ≈BU 508A			BU 2508 A	18j
ON 4147	Si-N	≈S 2000A, ≈BU 508A			BU 2508 A	18j
ON 4152	Si-N	≈S 2000A, ≈BU 508A			BU 2508 A	18j
ON 4213	Si-N	≈BUT 56A			BUT 56A	17j
ON 4223	Si-N+Di	≈BU 508D			BU 2508 D,DW	18j, 16j
ON 4302	Si-N	≈S 2000A, ≈BU 508A			BU 2508 A	18j
ON 4337	Si-N	≈BUT 11A			BUT 11 A	17j
ON 4341	Si-N	≈BUT 76A			BUT 76A	17j
ON 4359	Si-N-Darl+Di	≈BD 683			≈BD 683	
ON 4437	Si-N	TV-HA			BU 2508 A	18j
ON 4466	Si-N	≈BUZ 90A			≈BUZ 90A	
ON 4521	MOS-N-FET-e	≈BUZ 90			≈BUZ 90	
ON 4542	Si-N	≈BU 508A			BU 2508 A	18j
OP 160	Opto	LED			-	
OR 100	Diac	Ub=28...36V, Ib<0,1mA, Itsm=2A	31		BR 100/(DB3)	31
ORP 60	Opto	CdS Foto-Wdst./resistor			-	
OT 129	F-Thy+Di	≈BT 129			TD 3FP 800H	17f
OY 100	Si-Di	≈OY 101			BY 133	31a
OY 101	Si-Di	GI, Uni, 800V, 0,5A	34a		BY 133	31a
OY 102	Si-Di	≈OY 101: 400V	34a		BY 133	31a
OY 241	Si-Di	GI, Uni, 800V, 0,45A	34a		BY 133	31a
OY 1011	Si-Di	GI, Uni, 1000V, 0,6A	34a		BY 133	31a
OY 1011/3	Si-Di	≈OY 1011: 1,5A	31a		BY 255	31a
OY 1011/4	Si-Di	≈OY 1011: 0,95A	31a		BY 133	31a
OY 1021	Si-Di	≈OY 1011: 600V	34a		BY 133	31a
OZ....	Z-Di				Z-Diode ....V	31a

## P

P 2 N2222(A)	Si-N	=2N2222(A): 0,625W	7a		-	
P 2 N2907(A)	Si-P	=2N2907(A): 0,625W	7a		-	
P 6 KE6.8...440(A)	Z-Di	TAZ, 6,8...440V, 600W(1ms)	31a		-	
P 6 KE6.8...440C(A)	Z-Di	bidirektional/back to back	31a		-	
P 7 T-10...-110	Z-Di	TAZ, 10...110V, 700W(1ms)	31a		-	
P 7 T-...B	Z-Di	=P 7 T-...: bidirektional	31a		-	
P 80 C592 ...A	CMOS-μC-IC	8 Bit, 2x512B RAM, 0kB ROM, 80C51 CPU	68-PLCC		-	
P 80 CE528 ...	CMOS-μC-IC	8 Bit, 512B RAM, 0kB ROM, 80C51 CPU	-		-	
P 80 CE598 ...	CMOS-μC-IC	8 Bit, 2x256B RAM, 0kB ROM, 80C51 CPU	-		-	
P 83 C053	CMOS-μC-IC	≈80C51, TV, Video, 8192x8 mask. ROM	42-SDIP		-	
P 83 C524 ...A	CMOS-μC-IC	8 Bit, 512B RAM, 16kB ROM, 80C51 CPU	44-PLCC		-	
P 83 C524 ...P	CMOS-μC-IC	=P 83C524...A:	40-DIP		-	
P 83 C592 ...A	CMOS-μC-IC	8 Bit, 2x512B RAM, 16kB ROM, 80C51 CPU	68-PLCC		-	
P 83 CE528 ...	CMOS-μC-IC	8 Bit, 512B RAM, 32kB ROM, 80C51 CPU	-		-	
P 83 CE598 ...	CMOS-μC-IC	8 Bit, 2x256B RAM, 32kB ROM, 80C51 CPU	-		-	
P 83 CL167...168...	CMOS-μC-IC	8 Bit, Volt. Synth. Tuning, OSD, I°C	64-...		-	
P 83 CL267...268...	CMOS-μC-IC	8 Bit, Volt. Synth. Tuning, OSD, I°C	64-...		-	
P 87 C054	CMOS-μC-IC	≈80C51, TV, Video, 16384x8 OTPROM	42-SDIP		-	
P 87 C592 ...A	CMOS-μC-IC	8 Bit, 2x512B RAM, 16kB EPROM, 80C51	68-PLCC		-	
P 87 CE598 ...	CMOS-μC-IC	8 Bit, 2x256B RAM, 32kB EPROM, 80C51	-		-	
P 89 CE528 ...	CMOS-μC-IC	8 Bit, 512B RAM, 32kB EEPROM, 80C51	-		-	
P 90 CE201(AEB)	CMOS-μC-IC	16-Bit Single Chip Microcontroller,I°C	64-MP		-	
P 300 A....M	Si-Di	GI, 50...1000V, 5A(Tc=100°), 5μs	31a		BY 500/800	31a
P 511	Si-Di	=1N4007: 1300V	31a		BY 228	31a